



University of California, San Diego

ECE 164 – Analog Integrated Circuit Design

Project Report – Fall 2025

Huayu Zhang

PID: A69040187

Email: huz028@ucsd.edu

Futong Yang

PID: A69039862

Email: fuy003@ucsd.edu

Outline of Design

1. Design Methodology

This project employs the g_m/I_D methodology for core circuit size design. This method avoids the inaccuracies of traditional square-law formulas in short-channel technology (0.18 μm) and achieves precise control over power consumption, bandwidth, and stability.

In general, we divided the entire circuit into a bias circuit and an amplifier circuit, with two team members each responsible for one. Huayu Zhang was responsible for the amplifier circuit design, and Futong Yang for the bias circuit design. The g_m/I_D method played a significant role in the amplifier circuit design. We first decomposed the amplifier section into independent modules based on the function of each transistor, and then performed small signal analysis. Based on the calculation results, we could determine which parameters in the circuit directly affected various performance aspects. Using a lookup table, we could calculate the preliminary size of each transistor and estimate the required bias voltage for each node based on the project specifications. After performance testing of the amplifier circuit, the bias circuit could be designed accordingly.


For the bias circuit, first we used the ideal voltage source to bias the amplifying stages, after determining the exact DC operating points, magic battery is used to generate the same and precise gate voltage for them, which is less affected by PVT variation, only by adjusting the amounts of transistors working in triode region (or ratio k). For constant- g_m circuit, the PMOS constant- g_m bias circuit generates g_m for PMOS differential input (same length $L = 0.5\mu\text{m}$), minimizes power consumption by current scaling, and is less affected by PVT variation. The bias core generates I_{ref} by scaling mismatch ratio K between PMOS transistors M_{b1} and M_{b2} . This size difference forces a specific ΔV_{GS} across R_{bias} to set the reference current. Finally, adjust R_{bias} to control all current branches.

2. Power Optimization Strategy: Current Scaling


To minimize power dissipation while maintaining enough bandwidth and gain, we implemented a current scaling method. Instead of generating the full operating current within the bias circuit, we designed the Constant- g_m reference core to operate at a very low current level of 11.3 μA . This low-power reference is then mirrored to the main amplifier stages using precise ratios (scaling the MOSFET widths, W).

By decoupling the reference generation from the signal amplification, we ensured that most of the power budget is allocated to the signal path (Input Pair, Folded Cascode and Output Stage) to maximize transconductance g_m , rather than being wasted in the static bias branches. This approach allowed us to achieve a total power consumption of 1.18 mW, well below the 2.5mW specification. Next, we will explain how we manually calculated and made minor adjustments to each part of the circuit and finally compare the results of the manual calculations and simulations.

Components Values and Bias Currents

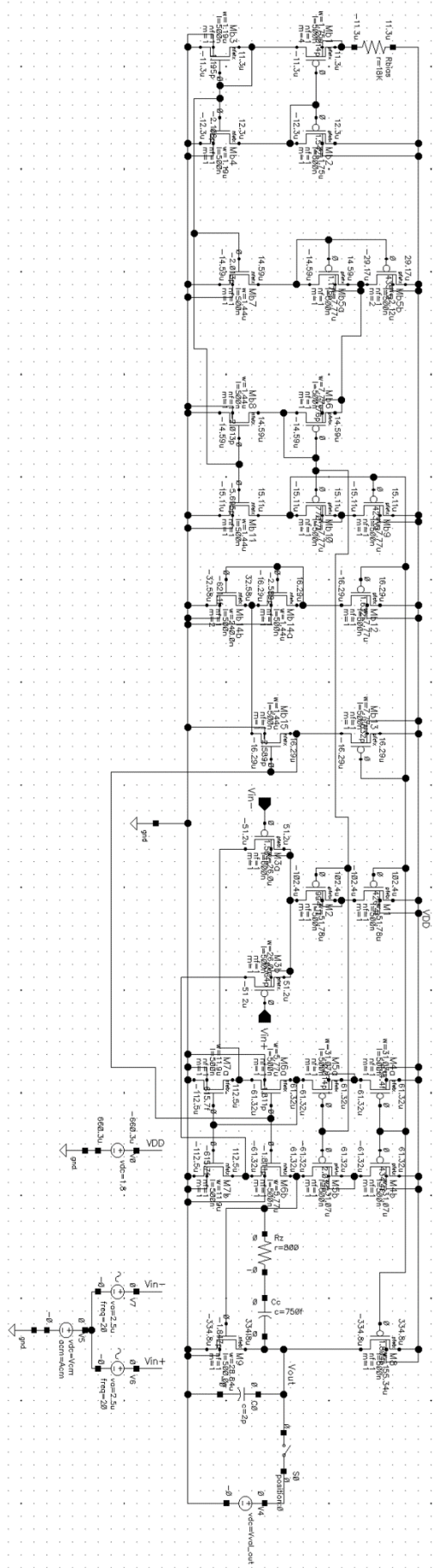

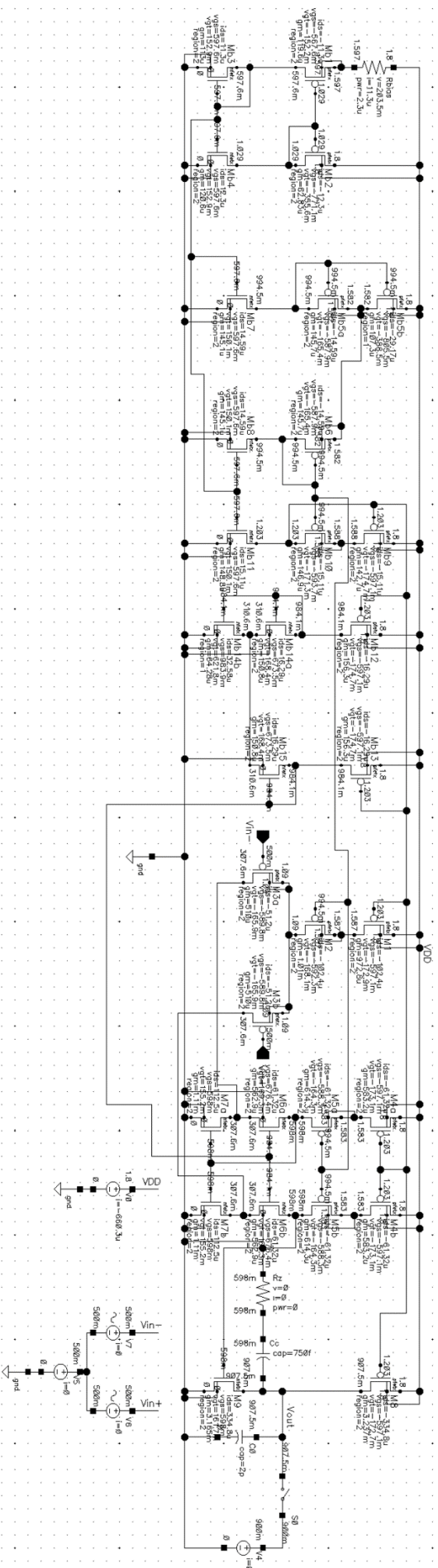
Gate Overdrive Voltages, Node Voltages and other DC Operating Points



Key Design Parameters Calculations

1. Hand Calculations

1.1 Two-stage amplifier circuit

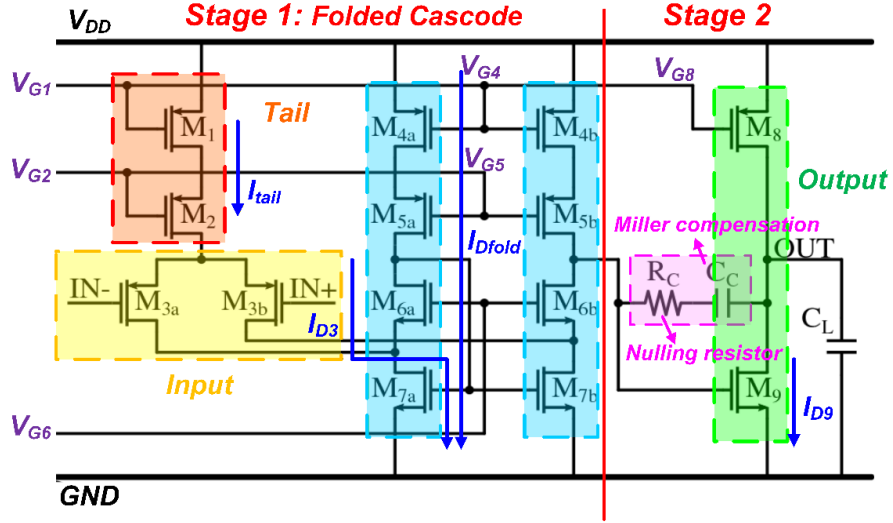

1.1.1 Small-signal gain analysis

First, we analyze Stage 1. With its half-circuit model, we can approximately get:

$$A_{v1} = -G_{m1} \times R_{o1} = -g_{m3} \times (R_{up} \parallel R_{down})$$

$$R_{up} \approx g_{m6} r_{o6} (r_{o7} \parallel r_{o3}) \quad R_{down} \approx g_{m5} r_{o5} r_{o4}$$

Similarly, for Stage 2:

$$A_{v2} = -G_{m2} \times R_{o2} = -g_{m9} \times (r_{o8} \parallel r_{o9})$$

Therefore, the total gain:

$$A_{vtot} = A_{v1} \times A_{v2} = g_{m3} [(g_{m6} r_{o6} (r_{o7} \parallel r_{o3})) \parallel (g_{m5} r_{o5} r_{o4})] \cdot [g_{m9} \times (r_{o8} \parallel r_{o9})]$$

To achieve a gain >70dB, experience suggests that Stage 1 typically provides high gain (50~70dB), while Stage 2 provides moderate gain (20~40dB).

1.1.2 Frequency response and poles & zeros

The parameters calculated in this part are crucial for satisfying UGBW and phase margin requirements. The dominant pole is located at the gate of M₉:

$$\omega_{p1} \approx -1 / R_{o1} R_{o2} G_{m2} C_C$$

with this equation, we can get the equation of UGBW:

$$UGBW \approx A_{vtot} \times \omega_{p1} = G_{m1} / C_c = g_{m3} / C_c$$

To meet $UGBW \geq 80\text{MHz}$, we can easily calculate the range of g_{m3} / C_c .

The secondary dominant pole is located at V_{out}, it determines the Phase Margin:

$$\omega_{p2} \approx -G_{m2}/C_L (1 + C_{par1}/C_C) \approx -g_{m9}/C_L$$

We can achieve this approximation by setting C_C to be much larger than the parasitic capacitance C_{par1} of stage 1. Considering the dominant pole, the Phase Margin = $90^\circ - \arctan(\omega_{0dB}/\omega_{p2})$. In order to guarantee a PM of 65° , it is required that $\omega_{p2} \geq 2.2 \times \text{UGBW}$. This determines the minimum value of g_{m9} .

Miller compensation introduces a right half-plane zero (RHP Zero), which degrades the phase margin:

$$\omega_Z = 1/C_C [(1/g_{m9}) - R_C]$$

By adjusting the nulling resistor R_C , we can either push this zero to ∞ ($R_C = 1/g_{m9}$) or let it cancel the secondary dominant pole. Our design chooses the former method.

1.1.3 Parameter calculation

- a) C_C : As mentioned above, we can set $C_C = 0.5C_L = 1\text{pF}$, which is large enough to suppress C_{par1} of Stage 1, while simplifying ω_{p2} .
- b) g_{m3} : In order to meet the project spec., $\text{UGBW} \geq 80\text{MHz}$, we use 90MHz for UGBW in our calculations. So $g_{m3} = 2\pi \times 90\text{MHz} \times 1\text{pF} = 565\mu\text{S} \Rightarrow 600\mu\text{S}$.
- c) g_{m9} : As mentioned above, we need $\omega_{p2} \geq 2.2 \times \text{UGBW}$ to meet the spec. for PM of 65° . To allow for adjustment, we can set $g_{m9} = 2\pi \times 2.5 \times 90\text{MHz} \times 2\text{pF} = 2.827\text{mS} \Rightarrow 3\text{mS}$.

1.1.4 I_D Budgeting

This part is the key to the g_m/I_D method, assigning I_D based on the function of each branch.

- a) Stage 1 input M_3 – pursuing high gain

Considering the project spec. for $V_{ov} \geq 150\text{mV}$, g_m/I_D needs to be smaller than 13.3 S/A . We can set g_{m3}/I_{D3} to be 12 S/A , so $I_{D3} = g_{m3}/(g_{m3}/I_{D3}) = 600\mu\text{S} / 12 \text{ S/A} = 50\mu\text{A}$. Then the current of tail $I_{tail} = I_{D1} = I_{D2} = 2I_{D3} = 100\mu\text{A}$.

- b) Folded cascode $M_4 \sim M_7$ – consider the swing

So we set $I_{Dfold} = 1.2I_{D3} = 60\mu\text{A}$ to prevent the transistors from slewing during signal swings. According to $g_m/I_D = 2/V_{ov}$, we can use 200mV for V_{ov} so that $g_{mfold}/I_{Dfold} = 10 \text{ S/A}$.

- c) Stage 2 output M_8, M_9 – responsible for driving load and ensuring output swing

To meet the spec. for output common-mode range $0.4 \sim 1.4\text{V}$, we need to set $V_{ov} \leq 400\text{mV}$. So, with $V_{ov} = 200\text{mV}$, $g_{m9}/I_{D9} = 2/V_{ov} = 10 \text{ S/A}$.

Then the current of output branch $I_{D8} = I_{D9} = g_{m9}/(g_{m9}/I_{D9}) = 3\text{mS} / 10 \text{ S/A} = 300\mu\text{A}$.

1.1.5 Sizing

In this section, we will use a lookup table in MATLAB provided by Professor Hall to find and calculate the transistor size based on the previously determined g_m/I_D .

First, we need to choose the L of the transistor, based on experience, choose $2x \sim 3x L_{min}$. $0.5\mu m$ is a good size with $L_{min} = 0.18\mu m$.

a) Stage 1 input PMOS M_3 : With $I_{D3} = 50\mu A$ and $g_{m3}/I_{D3} = 12 \text{ S/A}$, we can look up the corresponding $I_{D3}/W_3 = 1.2263$. Then $W_3 = I_{D3}/(I_{D3}/W_3) = 40.773\mu m$.

b) Tail PMOS M_1, M_2 : To make sure they are in saturation with $I_{tail} = 100\mu A$, we can set $V_{ov} = 200mV$. So the $g_{mtail}/I_{tail} = 10 \text{ S/A}$ and corresponding $I_{tail}/W_{tail} = 1.9312$. Then $W_{tail} = I_{tail}/(I_{tail}/W_{tail}) = 51.781\mu m$.

c) Folded cascode: PMOS $M_{4,5}$ and NMOS $M_{6,7}$

Similarly, with $I_{Dfold} = 60\mu A$, we can calculate and get $W_{4,5} = 31.07\mu m$ & $W_6 = 5.766\mu m$. As for M_7 , $I_{D7} = I_{Dfold} + I_{D3} = 110\mu A$, so $W_7 = 10.571\mu m$.

d) Stage 2 output M_8, M_9 : Similarly, $W_8 = 155.344\mu m$ and $W_9 = 28.84\mu m$.

1.1.6 DC & AC analysis: check DC Operating Point and specifications

As mentioned above, the g_m/I_D method cannot calculate the circuit operation very accurately. Therefore, we must make necessary adjustments to the calculated parameters based on SPICE simulation results. Before building the circuit for simulation and debugging, we need to roughly determine the gate voltage bias to be provided for each transistor in the circuit. Our preliminary calculation results are as follows:

$$V_{G1} = V_{DD} - V_{SG1} = 1.21V, V_{G2} = V_{DD} - V_{ov1} - V_{SG2} = 1.01V$$

$$V_{G8} = V_{G4} = V_{DD} - V_{SG4} = 1.21V, V_{G5} = V_{DD} - V_{ov4} - V_{SG5} = 1.01V$$

$$\text{Considering body effect, } V_{G6} = V_{ov7} + V_{GS6} = 0.8V \Rightarrow 1V.$$

To make sure each transistor is in sat., every $V_{ov} \geq 150mV$ and to meet all of the specs. in simulations, we made the following adjustments: $C_C \Rightarrow 0.75pF$, $W_3 \Rightarrow 26\mu m$. Clearly, using the g_m/I_D method made our work much more efficient in this project.

1.2 Bias circuit: Constant g_m bias & Magic battery

1.2.1 Constant g_m bias

$$R_{bias} = 2/g_{m,b2} (1 - 1/\sqrt{K})$$

Where K is the multiplicity and $K = 4$ in my project to simplify the hand calculation.

Therefore, $R_{bias} = 1/g_{m,b2}$. Targeting a low current $I_{ref} = 10 \mu A$ to save power, assume $V_{ov} = 200mV$ for M_{b2} so $g_m/I_D = 10 \text{ S/A}$ thus $g_{m,b2} = 100\mu S$. Finally, $R_{bias} = 10 \text{ K}\Omega$. Use the lookup table for current density $I_{Dp}/W_p = 1.9312$ then $W_p = 5.18\mu m$. Also, for the NMOS current mirror $I_{Dn}/W_n = 10.4061$, then $W_n = 0.96\mu m$. Use current scaling by mirrors to generate $I_{amp} = m \cdot I_{ref}$ for amplifying stages.

1.2.2 Magic battery

M_{b5a} and M_{b5b} provide bias voltage V_{G2} and $V_{G5} = V_{DD} - 2V_{ov} - |V_{tp}|$ with M_{b6} which is

around 1V. PMOS battery bias equation: $V_B = V_{DD} - (k+1)^{1/2} V_{ov} - |V_{tp}|$ so $k = 3$. The width of M_{b5a} is 3 times larger than M_{b5b} . Due to 2 branches of current flow through M_{b5b} , the multiplicity $m = 2$. The size of magic battery should be replica of amplifying stages.

In a similar way, M_{b14a} and M_{b14b} provide bias voltage $V_{G6} = 2V_{ov} + V_{tn} = 1V$ with M_{b15} . Also, the equation is $V_B = (k+1)^{1/2} V_{ov} + V_{tn}$ so $k = 3$. Width of M_{b14a} is 3 times larger than M_{b14b} . Due to 2 branches of current flow through M_{b14b} , the multiplicity $m = 2$. The size of magic battery should be replica of amplifying stages.

1.3 Power Dissipation & Key Design Parameters Comparison

$I_{tail} = I_{D1} = I_{D2} = 100\mu A$. $I_{Dfold} = I_{battery} = 60\mu A$ each branch. 2 folded cascode branches and 5 battery branches. Constant $g_m I_{ref} = 10\mu A$ each branch and $I_{D8} = 300\mu A$. Power = $V_{DD} \cdot I_{tot} = 1.512mW$ (Before current scaling to minimize the power in battery stage).


Para.	Calc.	Simu.	Para.	Calc.	Simu.	Para.	Calc.	Simu.
I_{ref}	10 μ	11.3 μ	R_{bias}	10k	18k	Pole ₁	12.5k	13.6k
$g_{m,b2}$	100 μ	62.83 μ	C_c	1p	0.75p	Pole ₂	238M	70M
V_{ov}	200m	165.9m	R_c	333.3	800	Zero	∞	500M
A_0 (dB)	90.6	76.92	I_{D8}	300 μ	334.8 μ	V_{G5}	1.01	0.995
UGBW	90M	86.9M	Power	1.51m	1.18m	V_{G6}	1.00	0.984

The hand-calculation value does not fully match the simulation value. First, for gate overdrive voltage V_{ov} , though we always assume $g_m/I_D = 2/V_{ov}$, this is not always the case in the real design because we did not consider velocity saturation and V_{DS} mismatch (in g_m/I_D method, assume $V_{DS}=0.9V$), which causes channel length modulation and drain-induced barrier lowering. Those effects affect V_{ov} (or V_{gt}), making the transconductance efficiency higher and affecting g_m even the output impedance r_o of each transistor, which leads to a large discrepancy in DC gain. Also, even if we consider body effect, it still affects the accuracy of results.



About the ratio in magic battery, for PMOS battery, its source is connected to body so no body effect theoretically, the ratio k is nearly 3 and multiplicity $m = 2$. However, for the NMOS battery, the real ratio $k = 6$, not 3 ($m = 2$). The body effect is one reason for it, but the main reason is the mismatch of current flows through battery and FC circuit.

Also, for the power, we changed the width of battery circuit and mirror bias. The limitation of decreasing power consumption is the “ m ” factor ≤ 20 . Theoretically, the ratio of current in the second stage and constant- g_m bias can be $20^3 = 8000$. Similarly, current in PMOS battery can be $20^2 = 400$ times smaller than the one in NMOS battery, which can significantly reduce the static power in biasing circuit while keeping a good gain and bandwidth.


Simulation Bode Plot

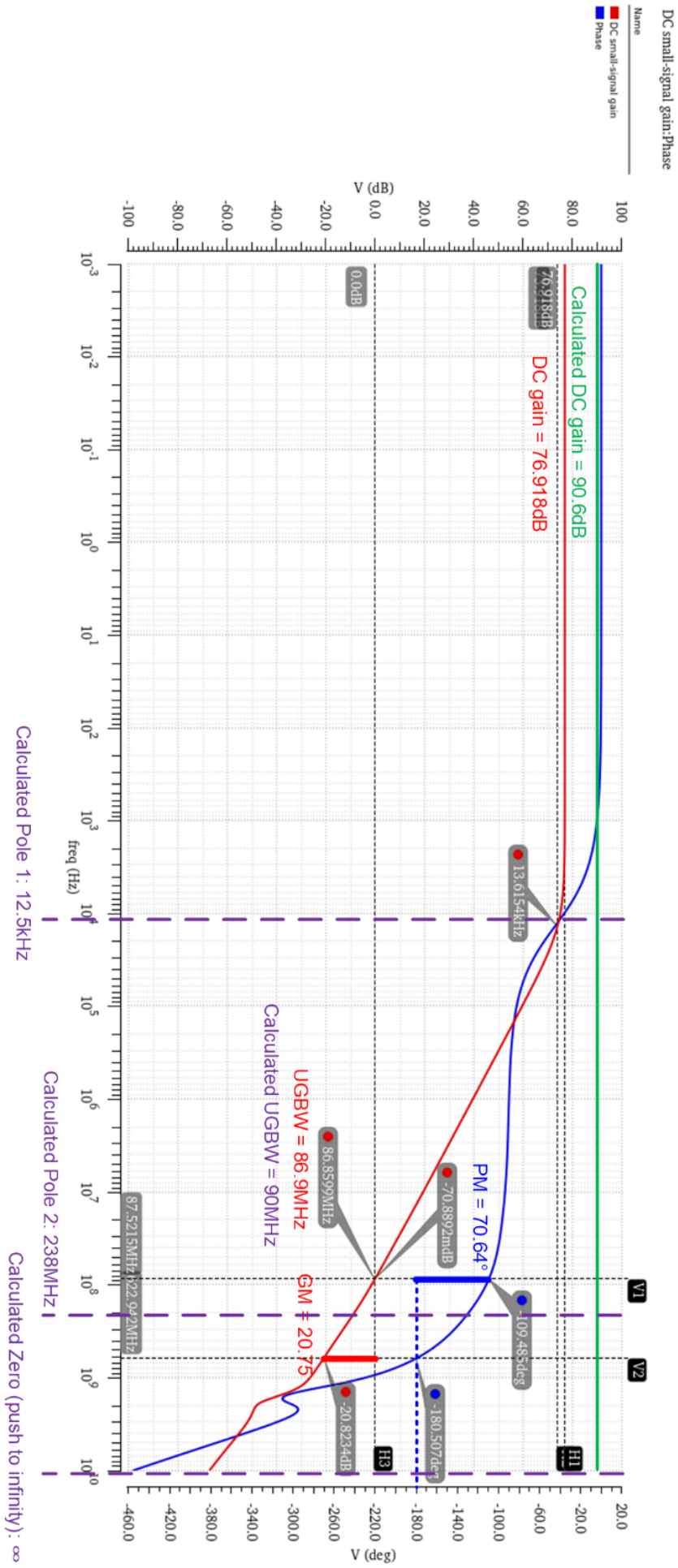

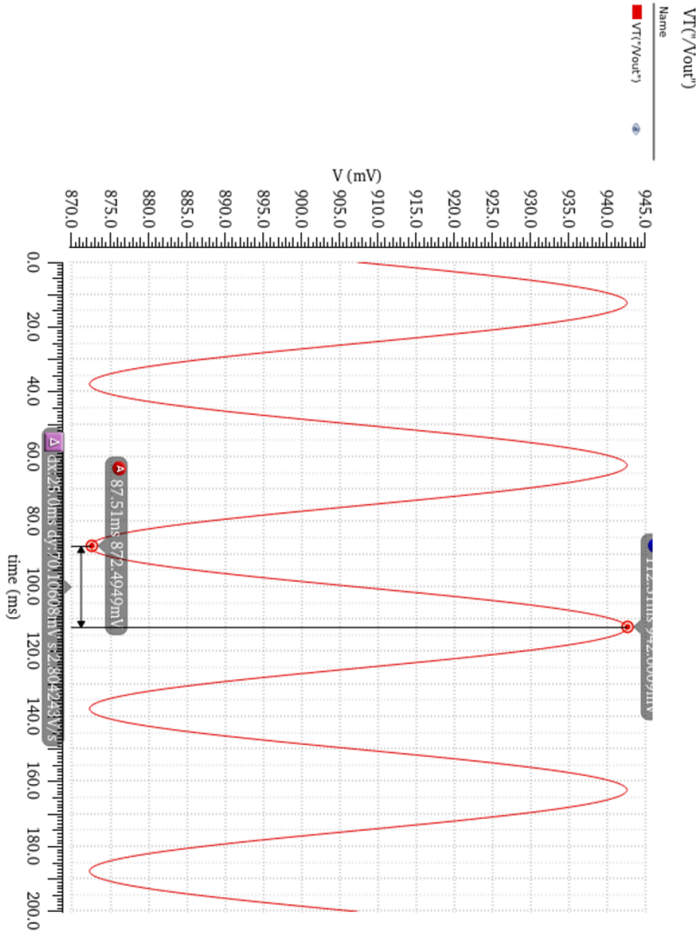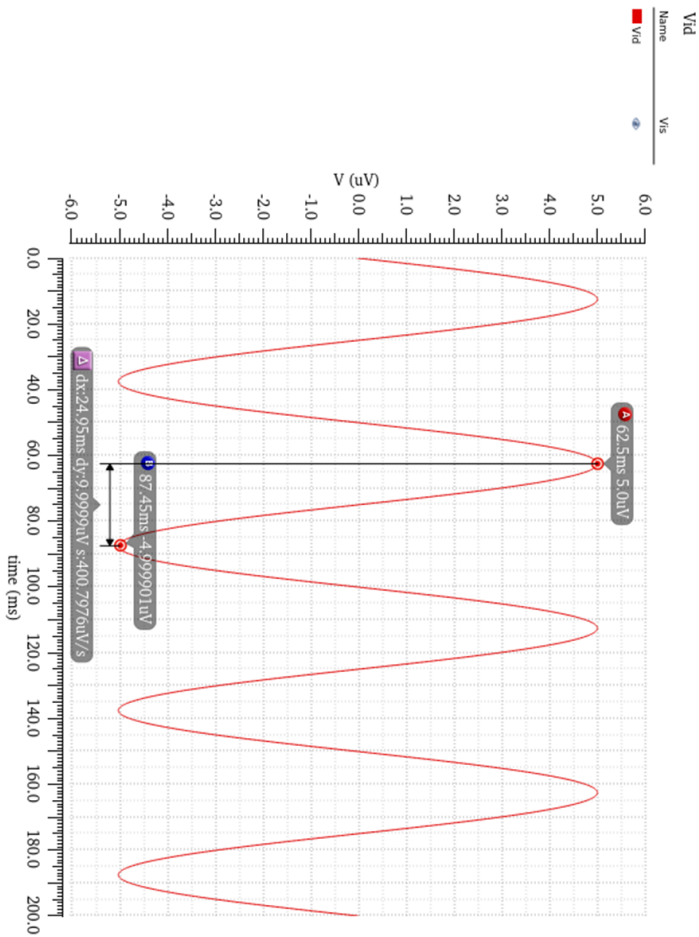
Transient simulation results for a $10\text{ }\mu\text{V}_{\text{pp}}$ sinusoid at 20 Hz



Input Common-mode Range

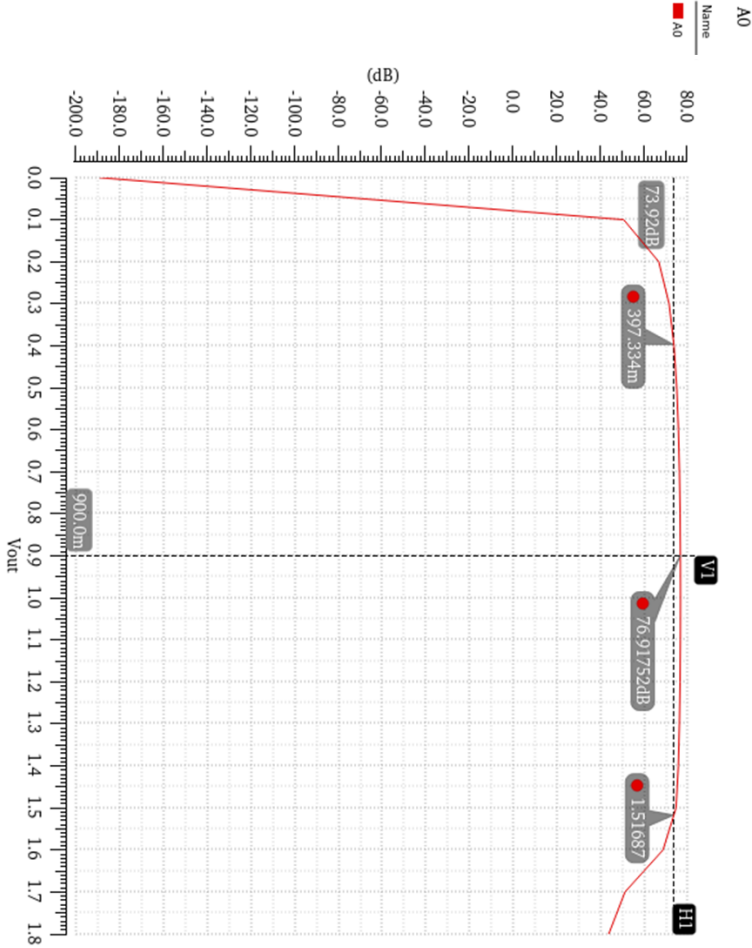

Output Common-mode Range

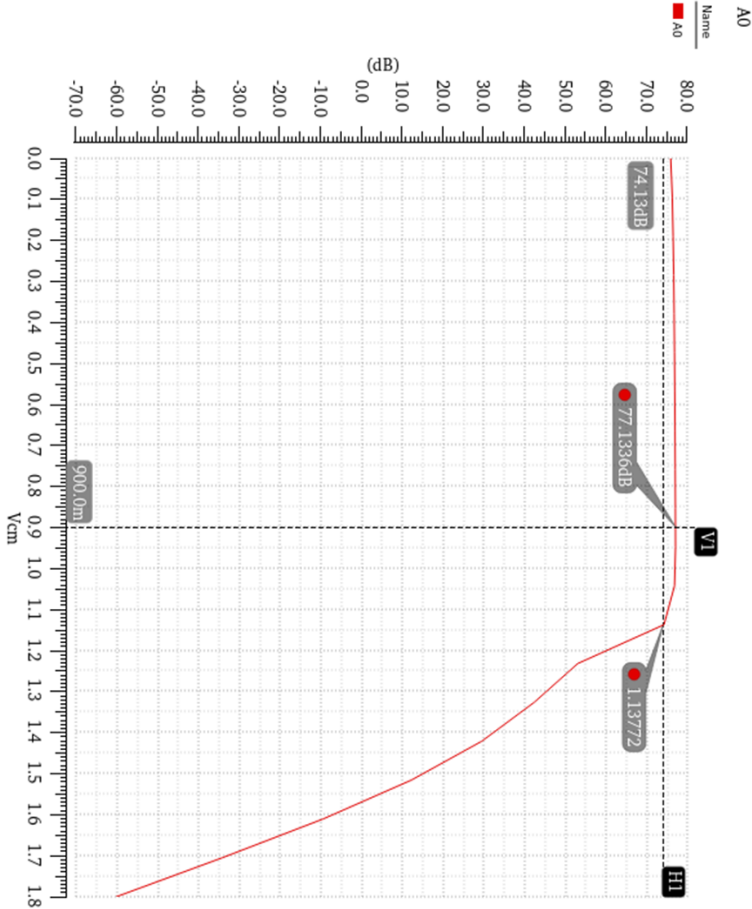

Comments and Conclusions

Finally, we completed the project and met each required specification, but at first, we used the square law to calculate everything because we did the same thing for previous homework. Right after the first simulation for those 2 amplifying stages with ideal bias, there were too many discrepancies between the hand-calculation results and SPICE model results. Therefore, we changed our strategy – using g_m/I_D method to make accurate assumptions and estimations, which decreased the workload of debugging in Cadence. However, we noticed that there are still some discrepancies between g_m/I_D and the SPICE model. The most troubling thing is the value of V_{ov} (V_{gt}), we assumed V_{ov} (V_{gt}) = 200mV but it is even below 150mV after simulation because of the discrepancy between the real BSIM model and g_m/I_D method, which drove us crazy. At last, we learned how to do more accurate start point estimation by plotting V_{gt} versus g_m/I_D to make sure the actual $V_{gt} > 150\text{mV}$ from a selected g_m/I_D .

We also achieved significant results in power consumption optimization, with total power consumption controlled at around 1.18mW, far below the upper limit of 2.5mW.

What impressed us most in this project was the exploration and use of the g_m/I_D method. Although there is still a gap between the manual calculation results and the actual simulation results, we have deeply appreciated the superiority of this method in improving design efficiency during the project. It greatly reduces the workload of debugging parameters in Cadence, meaning that most of the time we are clear-thinking circuit design engineers rather than spice monkeys who keep tuning parameters blindly.

Furthermore, we gained a profound understanding of the nonlinearity and highly challenging trade-offs inherent in analog circuits. The design process taught us that the parameters of analog circuits are highly coupled. For example, increasing W to improve OCMR may sacrifice GBW due to increased parasitic capacitance; reducing current to lower power consumption may cause a decrease in g_m , thus worsening the phase margin. The design process is a continuous search for the "sweet points" of these trade-offs.

Overall, this project is a relatively complete design project that we completed after three months of studying analog integrated circuits. Compared to the lab problems in our regular assignments, the project is more systematic and tests a holistic view and overall thinking of an analog circuit design engineer, which will be very helpful for our future careers.